

Circuit Analysis

Calculate. For each loop in the circuits below, use Kirchhoff's voltage law to determine any missing voltage values.

<p>(a)</p> <p>$V_s = 9\text{ V}$ $V_1 = 4\text{ V}$</p> <p>$V_2 =$ $V_2 = 5\text{ V}$</p>	<p>(b)</p> <p>$V_s = 9\text{ V}$ $V_1 = 18\text{ V}$</p> <p>$V_t =$ $V_t = 9\text{ V}$</p>
<p>(c) Hint: which loop should you do first?</p> <p>$V_s = 1.5\text{ V}$ $V_1 = 1.0\text{ V}$</p> <p>$V_2 = 0.5\text{ V}$ $V_3 = 0.5\text{ V}$</p>	<p>(d)</p> <p>$V_s = 1.5\text{ V}$ $V_1 = 1.2\text{ V}$</p> <p>$V_2 = 1.5\text{ V}$ $V_3 = 0.3\text{ V}$</p>

Calculate. For each loop in the circuits below, use Kirchhoff's current law to determine any missing current values.

<p>(a)</p> <p>$I_s = 4\text{ A}$ $I_1 = 4\text{ A}$</p> <p>$I_2 = 4\text{ A}$</p>	<p>(b)</p> <p>$I_s =$ $I_1 = 3\text{ A}$</p> <p>$I_t =$ $I_s = 1.5\text{ A}$</p> <p>$I_t = 1.5\text{ A}$</p>
<p>(c) Hint: which loop should you do first?</p> <p>$I_s =$ $I_1 = 6\text{ A}$</p> <p>$I_2 = 4\text{ A}$ $I_3 = 2\text{ A}$</p> <p>$I_s = 6\text{ A}$</p>	<p>(d)</p> <p>$I_s = 8\text{ A}$ $I_1 = 3\text{ A}$</p> <p>$I_2 = 2\text{ A}$ $I_3 = 3\text{ A}$</p>


SPH 3U – Electricity – Circuit simulation

Answer the questions below using the circuit simulation. No need to do any calculations!

<https://phet.colorado.edu/en/simulation/circuit-construction-kit-dc>

- 1) **Verify Ohm's law:** Use a voltmeter and an ammeter to find the current and voltage across a 6 ohm resistor in a simple circuit. Enter your results in the table below. Using your results, find an equation for voltage, current and resistance?

Voltage (V)	Current (I)	Resistance (Ohms)
3	0.5	6
6	1.0	6
12	2.0	6
18	3.0	6
24	4.0	6

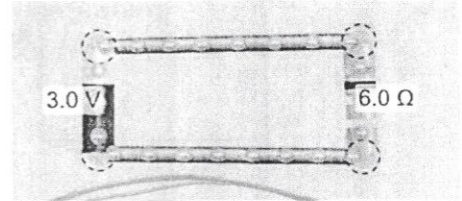






$V = IR$

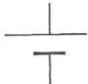- 2) Use a voltmeter and an ohmmeter to find the current and voltage across the resistors for the following circuits:
- A simple circuit: a 12 V battery connected to one 6 ohm resistor
 - A series circuit: a 12V battery connected to one 9 ohm and one 3 ohm resistor
 - A parallel circuit: a 12V battery connected to 6 ohm and 3 ohm resistors in parallel
 - A complex circuit: a battery with resistors in series and parallel




Draw your 4 circuits on the next page using the following symbols, find and label the voltage and the current across each resistor. Make conclusions based on your observations.

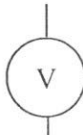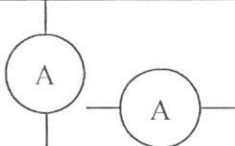 Battery	 Resistor	 wire	 Voltmeter	 Ammeter
--	---	---	---	--


- 3) Build the following circuit and determine all the unknown voltages, resistances and currents.

d) Fig.16.26

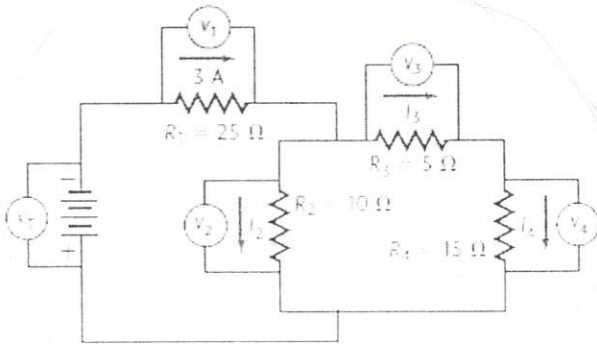


Name	V (V)	I (A)	R (Ω)
R ₁	75	3	25
R ₂	20	2	10
R ₃	5	1	5
R ₄	15	1	15
Total, R ₀	95 V	3	31.7

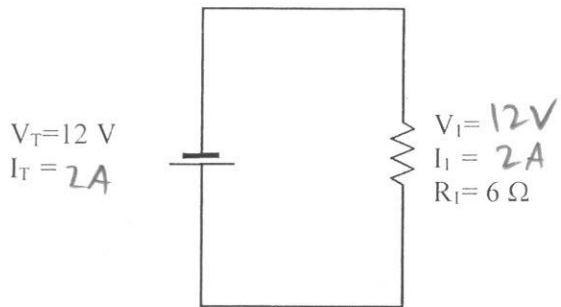3a) A simple circuit: a 12 V battery connected to one 6 ohm resistor.



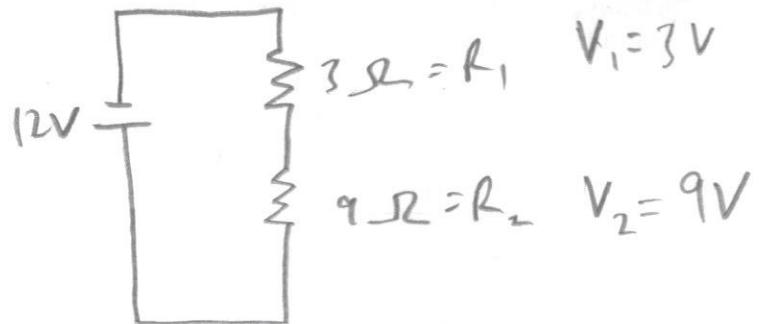3b) A series circuit: a 12V battery connected to one 9 Ω and one 3 Ω resistor



$$I_1 = I_2 = I_3 = 1\text{ A}$$

3c) A parallel circuit: a 12V battery connected to a 6 ohm and a 3 ohm resistors in parallel



$$V_1 = 12\text{ V} \quad V_2 = 12\text{ V}$$


$$I_1 = 1.33\text{ A} \quad I_2 = 4\text{ A}$$

$$I_T = 5.33\text{ A}$$

3d) A complex circuit: a battery with resistors in series and parallel


35. Determine all missing values. You might need to use other paper.

a) Fig.16.23

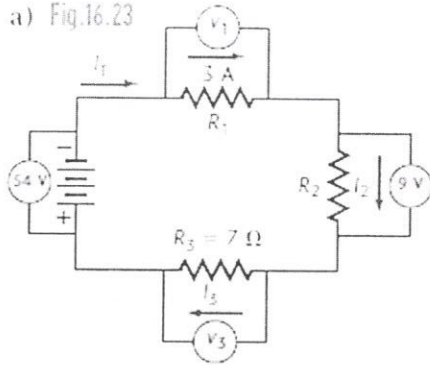


Name	V (V)	I (A)	R (Ω)
R ₁	24	3	8
R ₂	9	3	3
R ₃	21	3	7
Total, R ₀	54	3	18

b) Fig.16.24

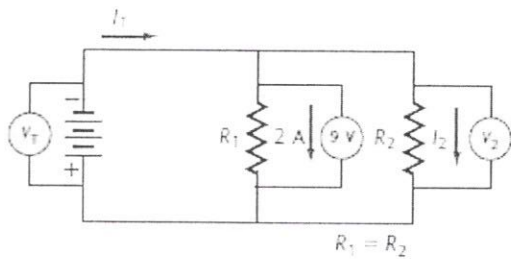


Name	V (V)	I (A)	R (Ω)
R ₁	9	2	4.5
R ₂	9	2	4.5
Total, R ₀	9	4	2.25

c) Fig.16.25

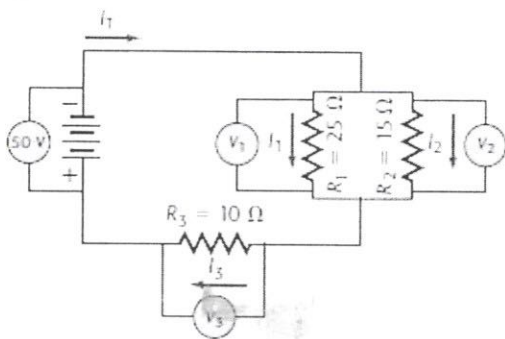

Name	V (V)	I (A)	R (Ω)
R ₁	24.2	0.97	25
R ₂	24.2	1.6	15
R ₃	25.8	2.6	10
Total, R ₀	50	2.6	19.4

d)

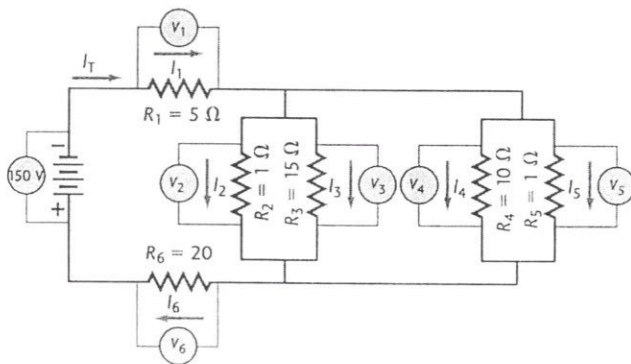

Name	V (V)	I (A)	R (Ω)
R ₁	29.5	5.9	5
R ₂	2.5	2.5	1
R ₃	2.5	0.17	15
R ₄	2.5	0.25	10
R ₅	2.5	2.5A	1
R ₆	118.8	5.9	20
Total, R ₀	150	5.9A	25.5