
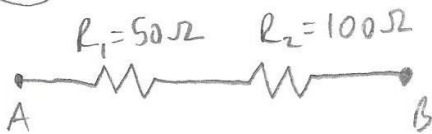


Find the equivalent resistance of each arrangement of resistors going from A to B


1.

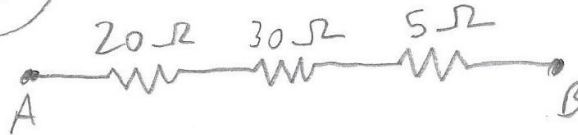


2.



3.

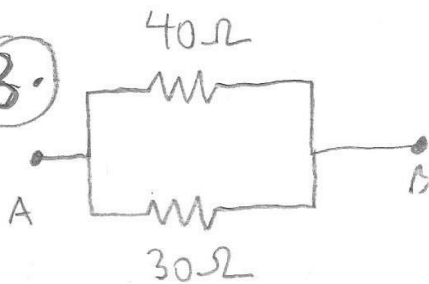


4.

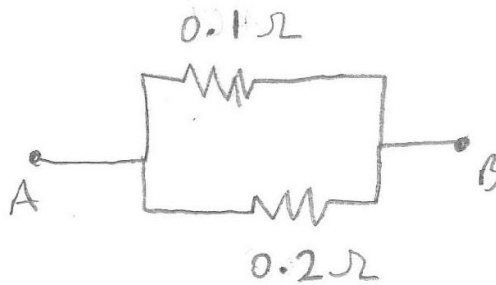


(answers...I think!)

1. $R_T = 150 \Omega$
2. $R_T = 55 \Omega$
3. $R_T = 17 \Omega$
4. $R_T = 0.07 \Omega$
5. $R_T = 65 \Omega$
6. $R_T = 77 \Omega$
7. $R_T = 31 \mu\Omega$
8. $R_T = 1.5 \text{ k}\Omega$


5.

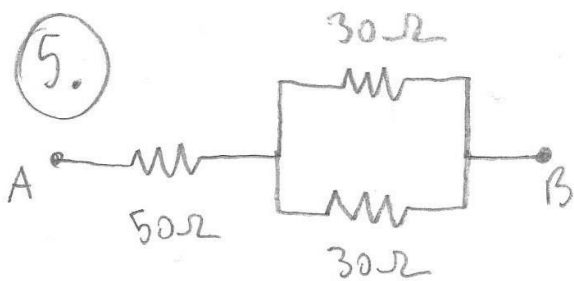


6.

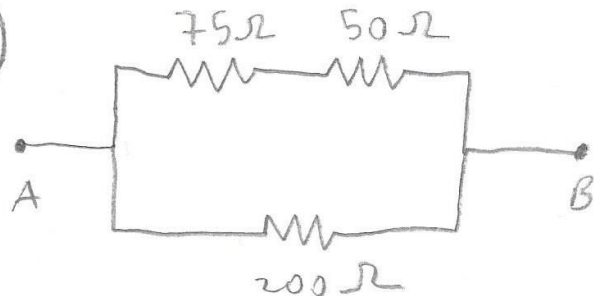

7.

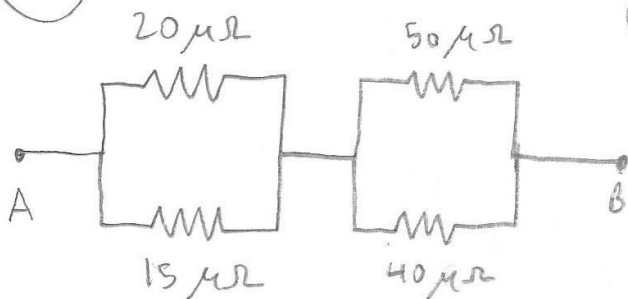

8.

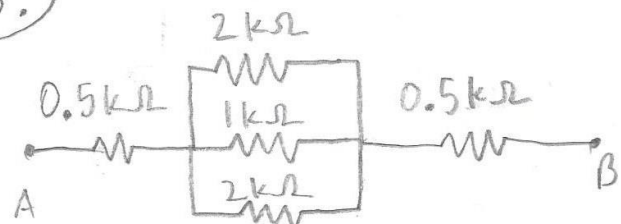

$\mu\Omega = \text{microohm} = 10^{-6} \Omega$